
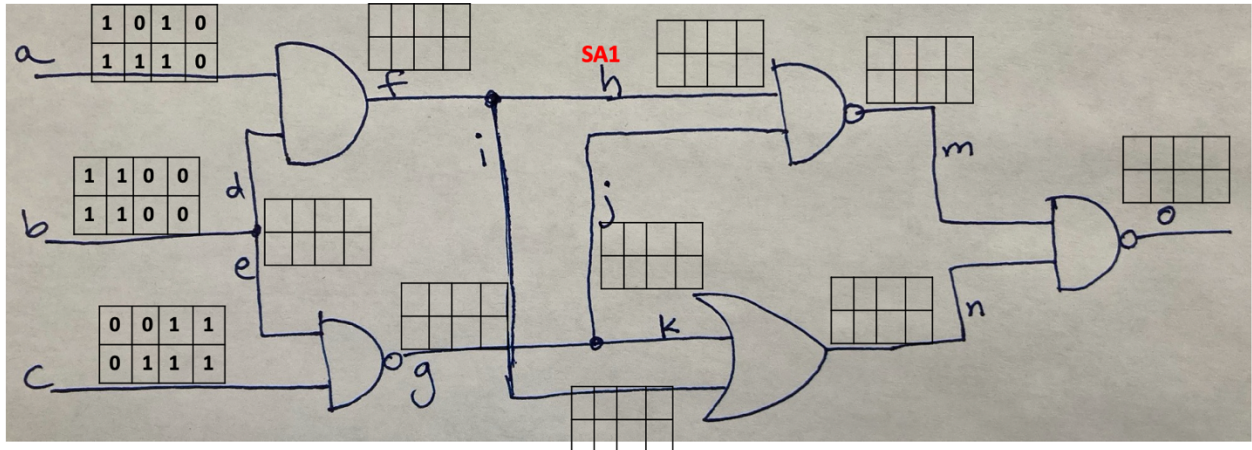


Homework # 4

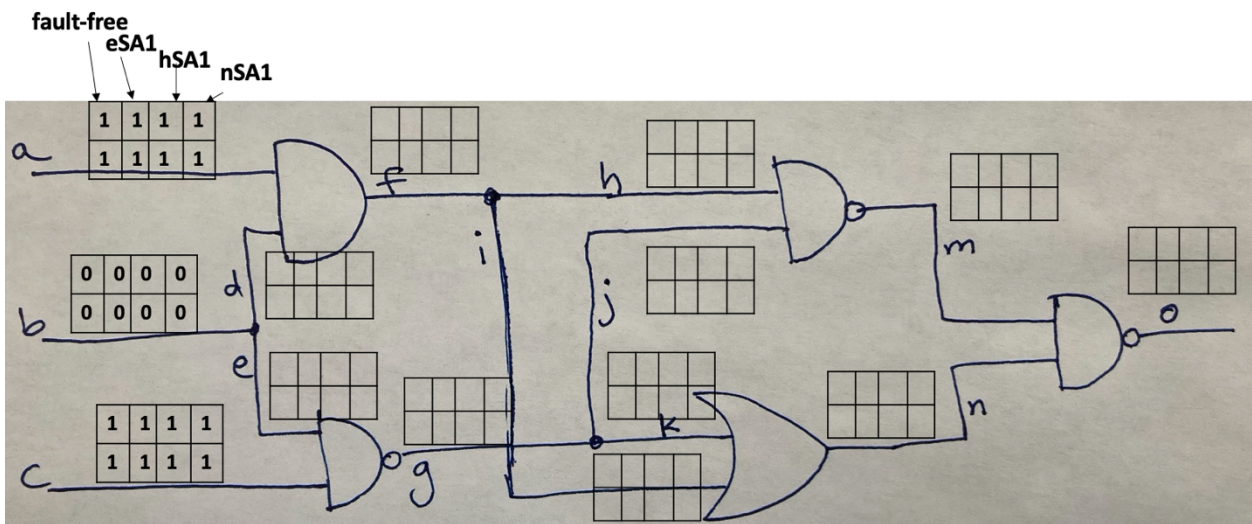- For the circuit shown below, perform Parallel Pattern Single Fault Simulation targeting the fault h stuck-at-1. You are given 4 vectors to simulate and the vectors are encoded as 11 for 1, 00 for 0 and 01 for U.



- For the circuit shown below, which is the same circuit as problem 1 but with different data, perform Parallel Fault simulation for the vector abc = 101 and three faults: e stuck-at-1, h stuck-at-1 and n stuck-at-1 to determine which faults will be detected at the primary output.



- For the circuit of Problem 1, perform deductive fault simulation to determine all faults that will be detected at the primary output 'o' for the test vector a=1 b=0 c=1.

